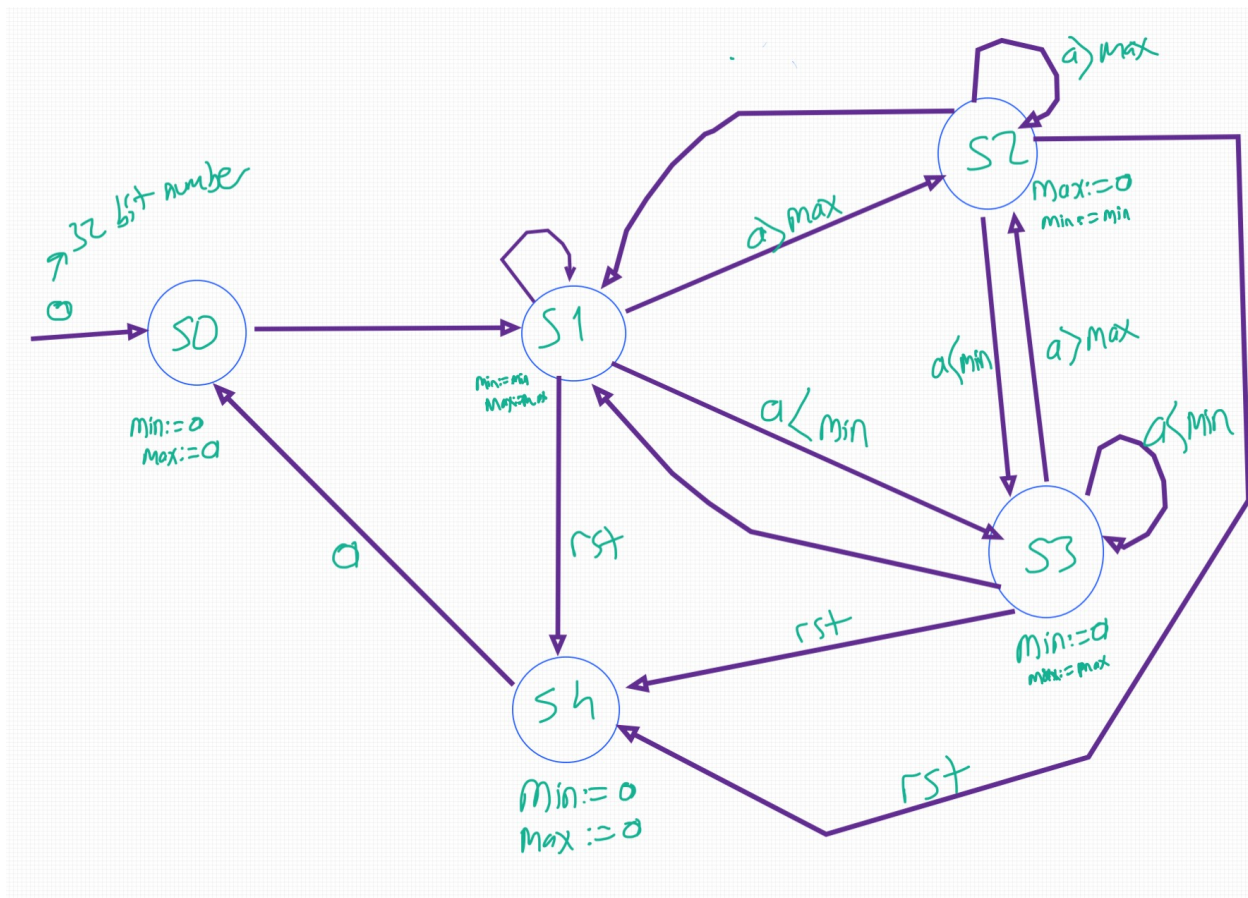


Student Name:Bilal Tekin

Student ID:2017400264

CMPE 240 Experiment 6 Preliminary Work


Step 1: Capture a High Level State Machine



Student Name:Bilal Tekin

Student ID:2017400264


Step 2: Construct a Datapath

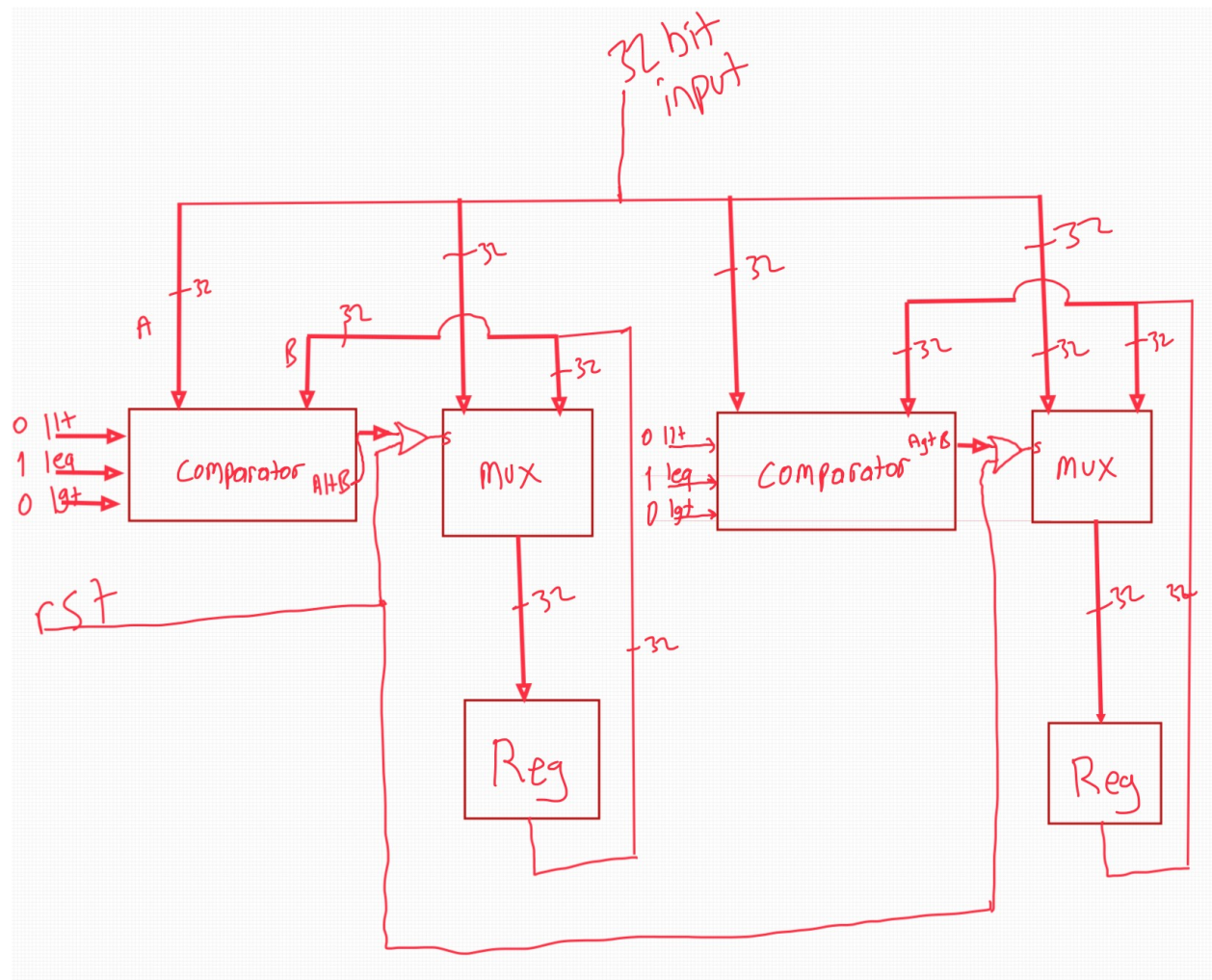

Student Name:Bilal Tekin

Student ID:2017400264

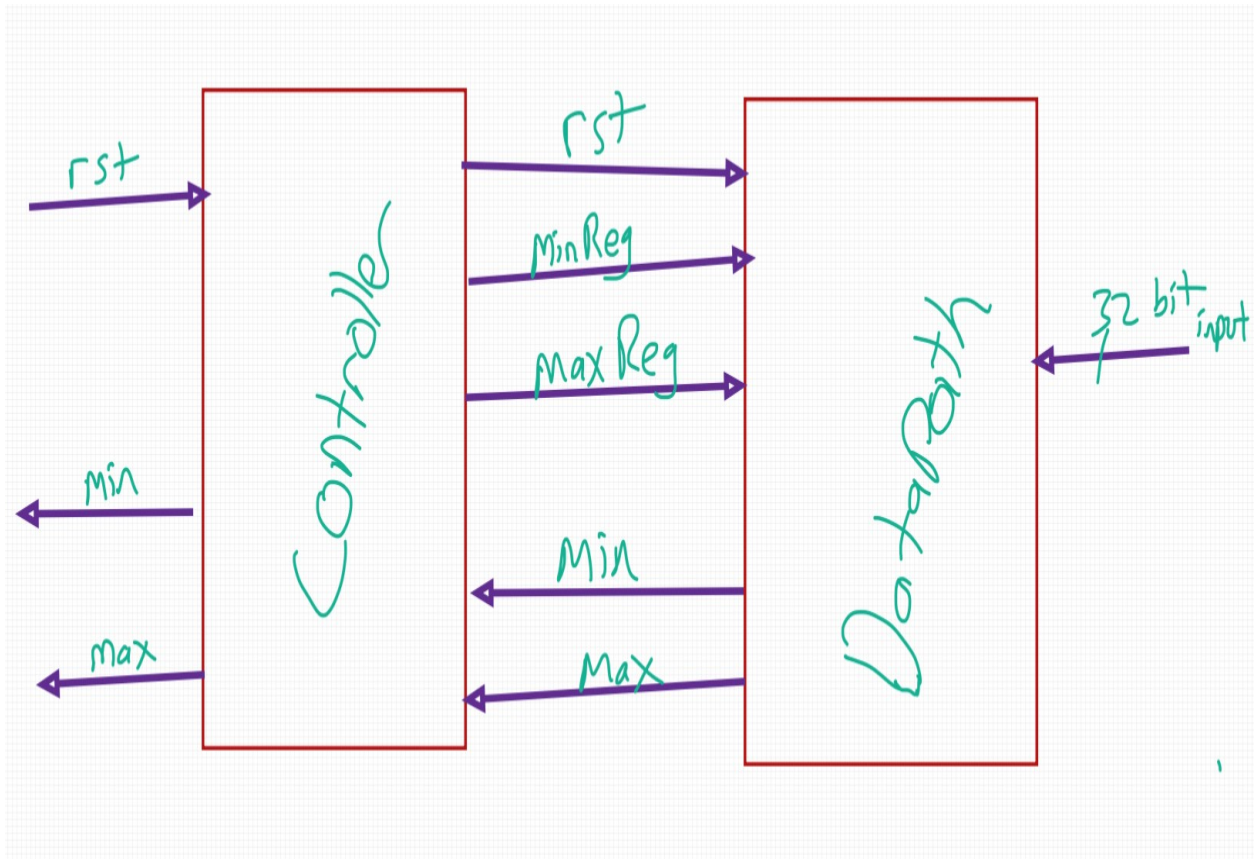Step 3: Connect the Datapath to a Controller



Student Name:Bilal Tekin

Student ID:2017400264

Step 4: Derive Controller FSM

